

Homework #3

#1 Three-Phase Definitions : $V_{LL} = 230 \text{ kV}$

$$a) V_{LN} = \frac{1}{\sqrt{3}} V_{LL} = \left(\frac{1}{\sqrt{3}}\right)(230 \text{ kV}) = 132.7906 \approx 132.8 \text{ kV}$$

$$b) V_{LL, \max} = \sqrt{2} V_{LL} = 325.27 \text{ kV}$$

$$c) V_{LN, \max} = \frac{\sqrt{2}}{\sqrt{3}} V_{LL} = \sqrt{2} V_{LN} = 187.7942 \text{ kV} \approx 187.8 \text{ kV}$$

#2 WYE & DELTA connections

$$Z_y = 20 \angle 30^\circ, V_{AN} = 100 \angle 0^\circ, V_{BN} = 100 \angle -120^\circ, V_{CN} = 100 \angle 120^\circ$$

This is a balanced Three-phase Y-connected system with positive-sequence sources.

$$a) I_A = \frac{V_{AN}}{Z_y} = \frac{100 \angle 0^\circ}{20 \angle 30^\circ} = 5 \angle -30^\circ$$

$$I_B = \frac{V_{BN}}{Z_y} = \frac{100 \angle -120^\circ}{20 \angle 30^\circ} = 5 \angle -150^\circ$$

$$I_C = \frac{V_{CN}}{Z_y} = \frac{100 \angle 120^\circ}{20 \angle 30^\circ} = 5 \angle 90^\circ$$

Line currents are also balanced, since they have equal magnitudes of 5 A & 120° displacement between any two phases

$$b) S_A = V_{AN} I_A^* = (100)(5) \angle 0 - (-30^\circ) = 500 \angle 30^\circ$$

$S_T = S_A + S_B + S_C = 3 S_A$ since we have balanced conditions the complex powers

$S_y = 3(500 \angle 30^\circ)$ delivered by b & c are identical to a.

$$S_T = 1500 \angle 30^\circ = 1500 (\cos(30^\circ) + j \sin(30^\circ)) = 1299 + j 750 \text{ VA}$$

$$c) I_{AB} = \frac{V_{AB}}{Z_\Delta} = \frac{\sqrt{3} V_{AN} \angle 30^\circ}{Z_\Delta} = \frac{(\sqrt{3})(100) \angle 30^\circ}{20 \angle 30^\circ} = 8.66 \angle 0^\circ \text{ A}$$

$$I_{BC} = \frac{V_{BC}}{Z_\Delta} = \frac{\sqrt{3} V_{BN} \angle -120^\circ + 30^\circ}{Z_\Delta} = \frac{(\sqrt{3})(100) \angle -90^\circ}{20 \angle 30^\circ} = 8.66 \angle -120^\circ \text{ A}$$

$$I_{CA} = \frac{V_{CA}}{Z_\Delta} = \frac{\sqrt{3} V_{CN} \angle 120^\circ + 30^\circ}{Z_\Delta} = \frac{(\sqrt{3})(100) \angle 150^\circ}{20 \angle 30^\circ} = 8.66 \angle 120^\circ \text{ A}$$

$$d) S_{AB} = V_{AB} I_{AB}^* = [(\sqrt{3})(100) \angle 30^\circ] [8.66 \angle 0^\circ] = 1499.956 \angle 30^\circ \text{ VA}$$

$$S_\Delta = S_{AB} + S_{BC} + S_{CA} = 3 S_{AB} = 3(1499.956 \angle 30^\circ) = 4499.868 \angle 30^\circ \text{ VA}$$

$$S_\Delta = 3897 + j 2249.934 \text{ VA}$$

$$e) S_{AB} = 1500 \angle 30^\circ = 3 V_{AB} I_{AB}^* = \frac{3 (V_{AB}) (V_{AB}^*)}{Z_{\Delta}^*}$$

$$Z_{\Delta}^* = \frac{[\sqrt{3} (100) / 30^\circ] [\sqrt{3} \cdot 100 \angle -30^\circ] \cdot 3}{1500 \angle 30^\circ} = 3 \cdot 20 \angle -30^\circ = 60 \angle -30^\circ$$

$$Z_{\Delta} = 60 \angle 30^\circ$$

#3 p.f. = .707 lagging

Power drawn = 240 kW

$V_{LL} = 440 \text{ V}$

$$a) |S| = \frac{P}{\text{p.f.}} = \frac{240 \text{ kW}}{.707} = 339.4625 \text{ kVA}$$

$$|I| = \frac{|S|}{\sqrt{3} V} = \frac{(339.4625 \text{ kVA})}{(\sqrt{3}) (440 \text{ V})} = 445.4290 \text{ A} = .445 \text{ kA per phase}$$

$$b) S_L = P + jQ = 240 + j(|S| \sin(\cos^{-1}(.707))) = 240 + j240$$

$$S_c = -j60$$

$$S_L + S_c = 240 + j240 - j60 = 240 + j180 = |S_{tot}| \angle \theta = 300 \angle 36.86^\circ \text{ kW}$$

$$|S_{tot}| = \sqrt{(240)^2 + (180)^2} = 300.1375$$

$$\theta = \tan^{-1}\left(\frac{180}{240}\right) = 36.86^\circ$$

$$\text{p.f.} = \cos(36.86^\circ) = .8 \text{ lagging}$$

c) We don't have to know whether it's a delta or wye connection because we have the power it consumes in total. Impedance would have to change.

#4 a) Three-phase motor draws 20 kVA at .707 p.f. lagging from a 220 V source

$$\cos \theta = \frac{P}{|S_m|}$$

$$P = |S_m| \cos(\theta) = (20 \text{ kVA})(.707) = 14.14 \text{ kW}$$

$$Q = |S_m| \sin \theta = (20 \text{ kVA}) \sin(\cos^{-1}(.707)) = 14.14 \text{ kVAR}$$

$$S_m = 14.14 + j14.14$$


$$S_{tot} = S_m + S_c = 14.14 + j14.14 - jX$$

$$S_{tot} = 14.14 + j(14.14 - X)$$

$$\cos \theta = .90 \text{ lagging}$$

$$\theta = \cos^{-1}(.90) = 25.84^\circ$$
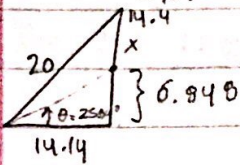
$$\theta = \tan^{-1}\left(\frac{14.14 - X}{14.14}\right)$$



$$(14.14)(\tan \theta) = 14.14 - X$$

$$14.14 \tan \theta - 14.14 = -X$$

$$-7.29 = 6.848 - 14.14 = -X$$

$$X = 7.29 \text{ kVAR}$$

b) Before Capacitors are added:

$$|I| = \frac{20 \text{ kVA}}{\sqrt{3} (220 \text{ V})} = 52.4 \text{ A}$$

After Capacitors are added:

$$S_{tot} = 14.14 + j6.848$$

$$|S_{tot}| = \sqrt{(14.14)^2 + (6.848)^2} = 15.71 \text{ kVA}$$

$$|I| = \frac{15.71 \text{ kVA}}{\sqrt{3} (220 \text{ V})} = 41.23 \text{ A}$$

5. Power Transfer Problem

$$Z = -j5\Omega = 5\angle -90^\circ$$

$$a) I = \frac{E_1 - E_2}{Z} = \frac{(100 \cos(0) + j(100) \sin(0)) - (100 \cos(30) + j100 \sin(30))}{5\angle -90}$$

$$I = \frac{100 - 86.6 - j50}{5\angle -90} = \frac{13.4 - j50}{5\angle -90} = \frac{51.76\angle -75}{5\angle -90} = 10.35\angle 15^\circ$$

$$S_1 = E_1(-I^*) = -(100)(10.35\angle -15^\circ) = -1035\angle -15^\circ = -1000 + j267.877$$

$$S_2 = E_2 I^* = (100)(10.35)\angle 30-15 = 1035\angle 15^\circ = 1000 + j267.877$$

Machine 1 consumes 1000 W, Machine 2 generates 1000 W

b) Machine 1 & 2 are both generating 268 VARs (see above for calculations)

$$c) \sum \text{generator convention} = \sum \text{Load convention}$$

$$Q_1 + Q_2 = -Q_L$$

$$268 + 268 = -Q_L$$

$$Q_L = -536 \text{ Var}$$

Load absorbs -536 VARs.

$$d) I_{\text{new}} = \frac{51.76\angle -75^\circ}{11.18\angle 63.43^\circ} = 4.629\angle -138.4^\circ$$

$$S_1 = -E_1(I_{\text{new}}^*) = (100)(-4.63\angle +138.4^\circ) = -463\angle 138.4^\circ = 346.04 - j307.4$$

$$S_2 = E_2(I_{\text{new}}^*) = (100)(4.63\angle 138.4^\circ) = 463\angle 138.4^\circ = -346.04 + j307.4$$

E_1 generates real power while E_2 absorbs it.

e) Machine 1 absorbs 307.4 vars & machine 2 generates 307.4 vars.

f) $Q_1 + Q_2 = -307.4 + 307.4 = 0$ vars ; Impedance absorbs 0 vars

g) Yes, the imaginary component of the impedance is positive so we know that there is an inductor present & it will consume VARs.

h) Reactive power is not paid for by consumers, so claiming that reactive power is being generated is misleading.