```
3.5 d) SBASE = 200 MVA VBASE = 16KV
      IBASE = 200 \times 10^6 \text{ VA} = 7216.88 \text{ A}
      E_1 = 24 \text{KV} / 16 \text{ KV} / 27.4^{\circ} = 1.5 / 27.4^{\circ} \text{ p.u.}
                                            MIC. 10 18 110 . ( (1 (6)) 1/2)
    T = \frac{V_{1}}{\sqrt{3}} - \frac{V_{2}}{\sqrt{3}} = \frac{.866 / 27.4^{\circ} - .5773^{\circ}}{j1.65} - \frac{.5773^{\circ}}{j1.65} = \frac{.1915 + j1.3935}{j1.65}
    I = .442/-25.67° = .267/-25.67° p.v.
                                                    James ( Carlo Carlo ) and
    I line = I. IBASE = (.267 /-25.67° p.v.) (7210.88 A) = 1933 /-25.67° A
    34-P= J3 VL IL cos (25.67°) = (J3)(16 KV)(1933) cos (25.67°) = 4.829 × 107 VI
    34-Q = J3 V_I, sin (25.67°) = (J3)(16 KV) (1933) sin(25.67°) = 2.320 x 107 VAR
    b) I rine, New = . 75 I rine = ( .75) 1933 ) (-25.67° = 144.975 (-25.67° A
       I Line, p.v. = 144.975/-25.67 A = .2/-25.67 A
7216.88
        I = ( ( 13 ) - ( \frac{14}{15} )
        I (jx) 11 7.577 8: 6-1.577 V.
       I(jx) +.577 VL= .577 E: L4
     (.2 (-25.67°) (1.65/90) +.577 = .577 & /4
          .33/64.3° +.577 = .577 Ei/4
       +.1429+j.2974+.577 = .577 & LY
              .7199 +j.2974 = -577 E; LY
             1.25 + 1.516 = 21 49
          1135 /22.39° = 8; /4
        Nan El = (1.35) (14 KV) = 21.0 KV
```

